

CIGRE
SESSION 2016

TUTORIAL


INTRODUCTION TO HVDC

Presented by: **Mojtaba Mohaddes**
SC B4

August 22, 2016




Presentation Layout

SESSION 2016
TUTORIAL 


- Advantages of HVDC
- HVDC Applications
- HVDC Technology
 - Line Commutated Converters
 - Voltage Sourced Converters
- Recent Developments
 - DC Grid
- Cigre Activities in HVDC

2

Advantages of HVDC

SESSION 2016
TUTORIAL 


Smaller towers

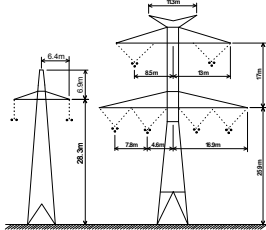


- HVDC towers are smaller and simpler than HVAC towers with similar transmission power rating

3

Advantages of HVDC

SESSION 2016
TUTORIAL 


Narrow right of way

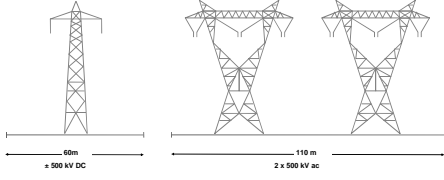


Typical transmission line right of way for 3000 MW if two ac towers are used

4

Advantages of HVDC


SESSION 2016
TUTORIAL 


- No need for Series or Shunt Compensation
- Controllable power flow
- Zero or no contribution to short circuit current



5

Advantages of HVDC


SESSION 2016
TUTORIAL 

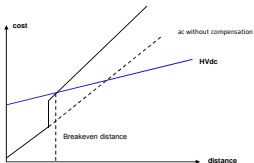

Comparison of capital cost for HVDC and HVAC

6

Advantages of HVDC

SESSION 2016
TUTORIAL 


AC cables are limited in length due to the charging current, HVDC cables have no length limitation

Typical charging currents for land cables*

Cross section (mm ²)	Current rating (A)	Charging current (A/km)
800	870	12.3
1000	960	13.7
1200	1115	15.1
1400	1205	15.9
1600	1280	16.6
2000	1410	17.6
2500	1540	19.2


* 500kV XLPE at 65C, flat formation

7

SESSION 2016
TUTORIAL 

Applications of HVDC

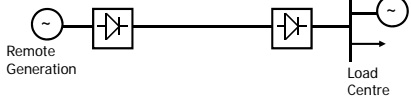
Transmission of bulk power from remote generation



Remote Generation


Load Centre

8

SESSION 2016
TUTORIAL 


Applications of HVDC

Long Distance Transmission

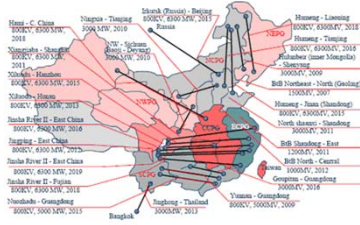


Examples of long distance HVDC in China

9

SESSION 2016
TUTORIAL 


Applications of HVDC

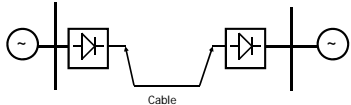Submarine or Underground Cable Transmission




Cable

10


SESSION 2016
TUTORIAL 

Applications of HVDC

HVDC Submarine Cables




11

SESSION 2016
TUTORIAL 


Applications of HVDC

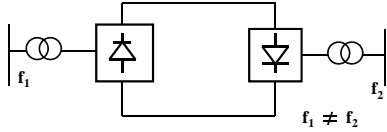Connecting Systems with Different Frequencies




$f_1 \neq f_2$

12

SESSION 2016
TUTORIAL 

Applications of HVDC


Connecting Systems with Different Frequencies




Argentina-Brazil HVdc interconnect

13

Applications of HVDC

SESSION 2016
TUTORIAL 

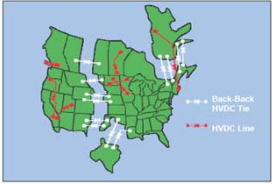
Connecting asynchronous systems with the same frequency



Connections between US east, west and Texas systems

34


Applications of HVDC

SESSION 2016
TUTORIAL 

- Moving large amounts of power over long distances.
- Moving power by cable over moderate to long distances.
- Moving power between asynchronous systems.
- Forcing power into an area (e.g. loop flow).
- Congested corridors
- Limiting short circuit currents through system segmentation.




35




Types of HVdc Converters

SESSION 2016
TUTORIAL 

- Line Commutated Converters (LCC) Using Thyristor Valves
- Voltage Source Converters (VSC) Using Insulated Gate Bipolar Transistors (IGBT)

36

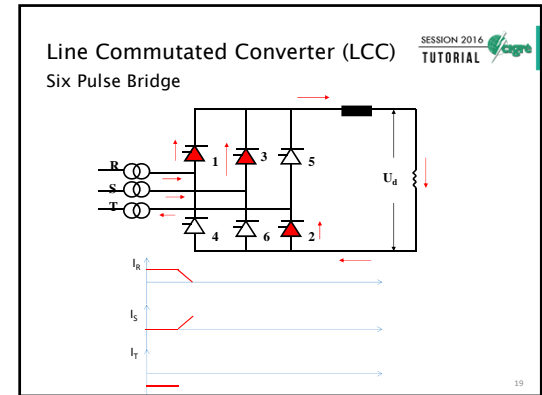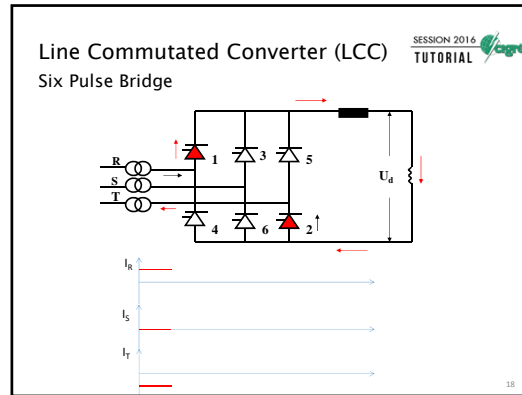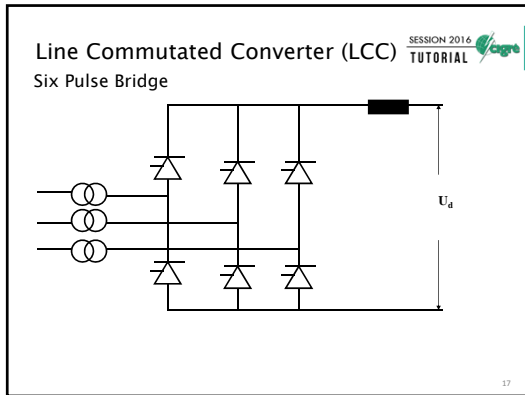

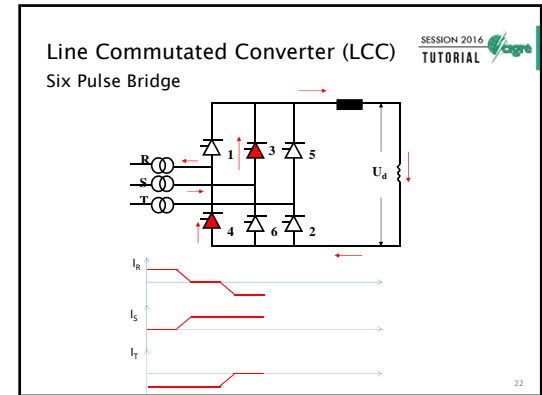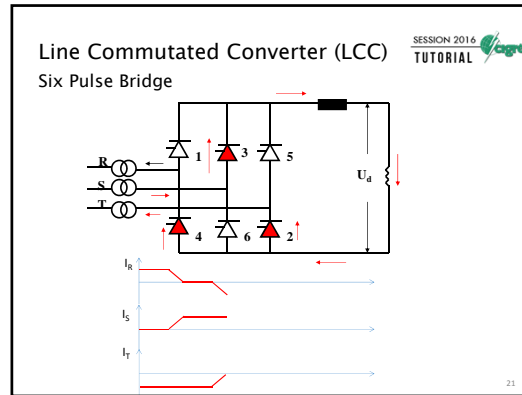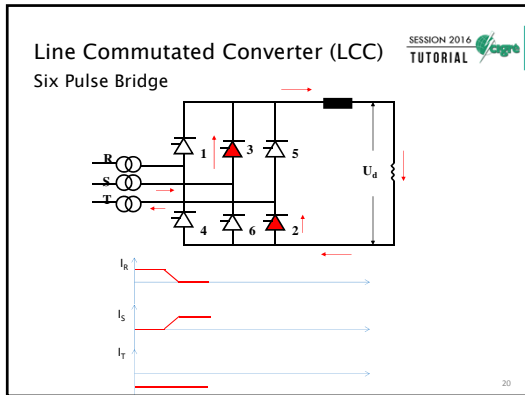

Line Commutated Converter (LCC) SESSION 2016 TUTORIAL

Six Pulse Bridge

AC Current Waveforms

- Currents are not sinusoidal
- Currents lag voltages (converter consumes reactive power)

23

Line Commutated Converter (LCC) SESSION 2016 TUTORIAL

Rectifier Wave Forms

Rectifier Wave Forms

24

Line Commutated Converter (LCC) SESSION 2016 TUTORIAL


Inverter Wave Forms

Inverter Wave Forms

25

Line Commutated Converter (LCC) SESSION 2016 TUTORIAL

Current Harmonics




The characteristic harmonics in the output current are of the order $6n \pm 1$
 where $n = 1, 2, 3, 4, \dots$
 The harmonics generated are of the order 5, 7, 11, 13, 17, 19,
 $I_n = \sqrt{6} I_d / n \pi$

26

Line Commutated Converter (LCC) SESSION 2016 TUTORIAL

Harmonics

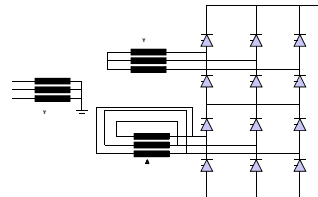


- 12 Pulse arrangement removes 5, 7, 17, 19, ... harmonics from AC currents
- Remaining current harmonics are of order $12n \pm 1$
- Remaining DC voltage harmonics are of order $12n$

27

Line Commutated Converter (LCC) SESSION 2016 TUTORIAL

Filters

- AC Harmonic filters also supply reactive power consumed by the converter



28

SESSION 2016
TUTORIAL

Line Commutated Converter (LCC)

Inverter Commutation Failures

- Commutation failures are the result of the incoming valve failing to take over the current, or re-fire of the outgoing valve. Commutation failures are due to:
 - AC system faults & disturbances
 - DC faults or disturbances
 - Equipment failures

29

SESSION 2016
TUTORIAL

Line Commutated Converter (LCC)

AC System Strength

$$\text{Short Circuit Ratio (SCR)} = \frac{\text{System MVA (S)}}{\text{DC Power (P}_{dc}\text{)}}$$

$$\text{Effective Short Circuit Ratio (ESCR)} = \frac{\text{System MVA (S)} - \text{Capacitive MVAR (Q}_c\text{)}}{\text{DC Power (P}_{dc}\text{)}}$$

- LCC requires certain level of ESCR, particularly at inverter


30


SESSION 2016
TUTORIAL


HVDC Configurations

Two Terminal Mono-polar System Ground Return

31

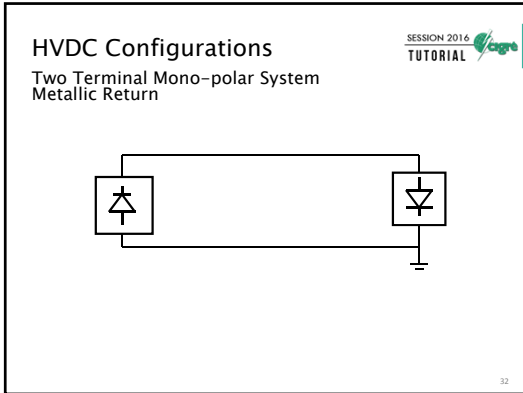

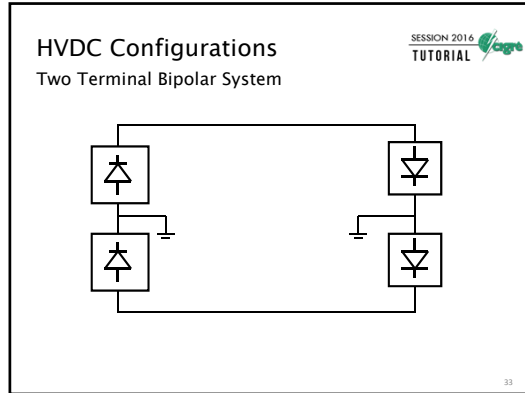

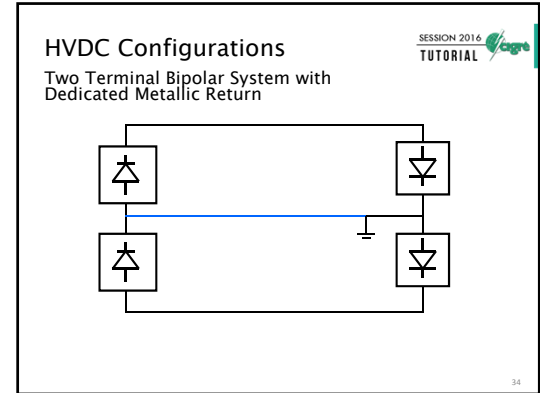


Line Commutated Converter (LCC) SESSION 2016 TUTORIAL

Available rating


- LCC converters are available up to 5kA and 800kV (DC); 1100kV systems may become available in the near future



35

Voltage Sourced Converters (VSC) SESSION 2016 TUTORIAL

Fundamentals

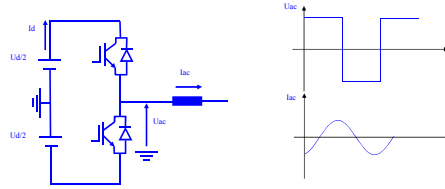


• Current path during the four quadrants

36

VSC Fundamentals SESSION 2016 TUTORIAL


Half bridge

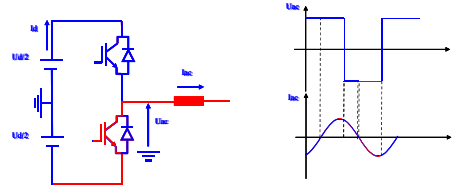


• Current path during the four quadrants

37

VSC Fundamentals
Full bridge


SESSION 2016
TUTORIAL 

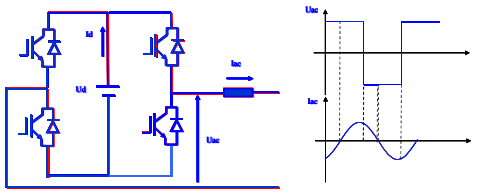

• Current path during the four quadrants

38


VSC Fundamentals


SESSION 2016
TUTORIAL 

- Problems with the simple converter:
 - Low power rating
 - Harmonic voltages $V_n = (\sqrt{2}/2n\pi)U_d$
 - Fixed relation between AC and DC voltages ($U_{ac} = 1.56U_d$)
 - not suitable for HVDC transmission

39

Multi-Module VSC
Operation Principles

SESSION 2016
TUTORIAL 

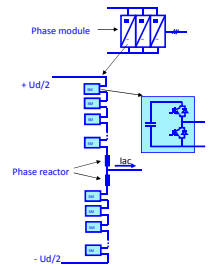

- Each arm contains N submodules
- SM Capacitor voltages are kept almost equal, $U_c = U_d/N$
- Each SM can be either OFF or bypassed (lower IGBT triggered, zero voltage at terminals) or ON (upper IGBT triggered, capacitor voltage at terminals)
 - $n_u = (N/2)(1 - m \cdot \sin(\omega t))$,
 - $n_l = (N/2)(1 + m \cdot \sin(\omega t))$
 - $V_{ac} = (U_d/2) \cdot m \cdot \sin(\omega t)$

40

SESSION 2016
TUTORIAL

Multi-Module VSC Operation Principles

- Modulation index m determines the magnitude of the ac voltage
- $V_u = U_c (N/2)(1 - m \cdot \sin(\omega t)) = U_d/2 - V_{ac}$
- $V_l = U_c (N/2)(1 + m \cdot \sin(\omega t)) = V_{ac} - U_d/2$
- At each moment total of N submodules are ON in each phase

41

SESSION 2016
TUTORIAL

Multi-Module VSC Modulation Techniques

- Nearest Level Control:
 - reference voltage is compared with fixed levels, every time it crosses a level a sub-module is turned on or off

42

SESSION 2016
TUTORIAL

Multi-Module VSC Modulation Techniques

- Level shifted PWM

43

SESSION 2016
TUTORIAL

Multi-Module VSC Modulation Techniques

- Phase shifted PWM

The figure contains three sub-graphs. The top graph shows a sinusoidal reference voltage U_{ref} and four phase-shifted triangular carriers labeled 'carriers N=4'. The bottom-left graph shows the resulting phase-shifted PWM signals $u_{pwm,ref}$ (p.u.) over time t . The bottom-right graph shows the resulting DC voltage U_{dc} (kV) over time t , which is a smoothed sinusoidal wave.

44

SESSION 2016
TUTORIAL

VSC Application HVDC Transmission

The diagram shows two AC systems, Sys2 and Sys1, connected via two VSC stations, VSC2 and VSC1. Each VSC station is connected to its respective AC system through a transformer.

- Similar to conventional HVDC, one station controls DC current and one station controls DC voltage
- Power reversal is through change of DC current direction, DC voltage polarity remains unchanged
- Reactive power is controlled independently at each terminal
- Can use XPLE cables (available up to 525kV)

45

SESSION 2016
TUTORIAL

VSC-HVDC Transmissio Symmetrical Monopole Configuration

The diagram shows two AC systems, Sys2 and Sys1, connected via two VSC stations, VSC2 and VSC1. Each VSC station is connected to its respective AC system through a transformer. Two high-voltage cables connect the VSC stations, with voltages labeled $+U_d/2$ and $-U_d/2$.

- Regular AC transformer
- Dc to ground fault does not cause high short circuit current
- Uses two high voltage cables, each rated for $U_d/2$
- Can be realized with half bridge converters without extra equipment
- No power transfer capability with a monopole outage

46

SESSION 2016
TUTORIAL

VSC – HVDC Transmission

Bipolar Configuration

- Can have ground or metallic return
- Converter transformer (dc stress on secondary windings)
- Dc to ground fault cause high short circuit current affecting ac systems (worse than LCC)
- Uses two high voltage conductors and possibly one low voltage conductor
- Can be realized with half bridge or full bridge converters, in case of HB requires extra equipment for dc and ac fault
- 50% (or more) power transfer capability with a monopole outage

47

SESSION 2016
TUTORIAL

Symmetrical Monopole

Ground Reference

- In symmetrical monopole configuration dc circuit is floating and therefore can drift.

using voltage divider resistors to prevent DC Voltage shifting

48

SESSION 2016
TUTORIAL


Symmetrical Monopole

Ground Reference

DC voltage balancing using star point reactor


- Required only at one station (except for STATCOM operation with DC cable disconnected) to avoid zero sequence current (mainly 3rd harmonic) circulation between stations
- Under normal conditions current in L1 is negligible ($L1 \gg \gg$)
- The voltage across R2 is equal to ΔU
- Stresses during dc line to ground fault should be considered in selection of R2

49


SESSION 2016
TUTORIAL 

MMC VSC Phase Reactors

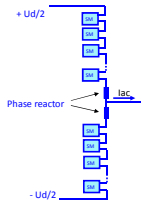
- Limits balancing currents between phases.
- Limits rate of rise for various fault currents




50

SESSION 2016
TUTORIAL 

MMC VSC Converter Charging

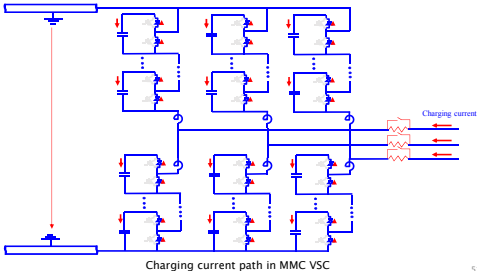

51

SESSION 2016
TUTORIAL 

MMC VSC Charging Resistor

- At the start up converter capacitors and dc cable are charged through diodes before deblocking
- A pre-insertion (charging) resistor is used to limit the charging current. The resistor is bypassed once the charging is complete
- For HB converter at the end of passive charging the sum of capacitor voltages in each arm is approximately equal to peak line to line voltage, i.e.

$$U_c = \sqrt{2} V_{LL} / N$$
- This is below the nominal capacitor voltage
- Passive charging is normally followed by active charging to raise capacitor voltages

52

SESSION 2016
TUTORIAL

MMC VSC Circulating Current

- Caused by the varying capacitance of the arms
- Mainly consists of 2nd harmonic

53

SESSION 2016
TUTORIAL

MMC VSC Circulating Current Suppression- AC filter

HVdc Light G4



54

SESSION 2016
TUTORIAL

Fault Performance AC Faults

- AC current is limited to 1pu by control action (reduced modulation index)
- For nearby faults current may be ordered to zero to minimize fault current contribution from converter
- For remote faults reduced amount of power will be delivered
 - This is superior to LCC behavior where a 10-15% voltage drop at inverter will cause commutation failure and interruption of power transmission
- Fault recovery is generally faster than LCC

55

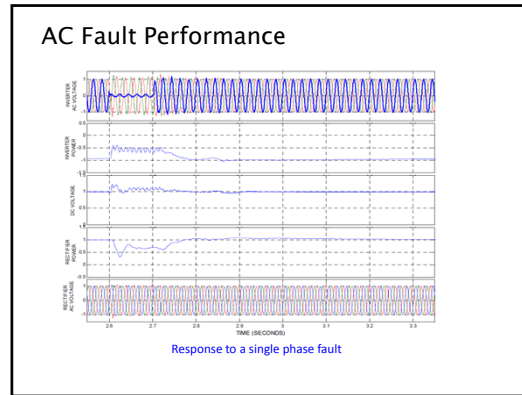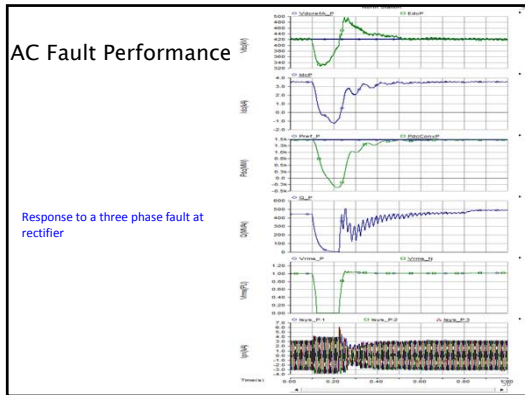




Fault Performance


SESSION 2016
TUTORIAL

Pole to ground fault in symmetrical monopole with HB (no dc breaker)

- Will cause sudden discharge of cable
- Will cause overvoltage on the healthy conductor
- Will be detected and cause blocking of all sub-modules; a trip signal is issued at the same time
- After blocking the pole-pole dc is determined by diodes only (limited to peak phase-phase voltage)
- Normally cleared by opening ac breakers at both ends, can restart after discharging the cable

58

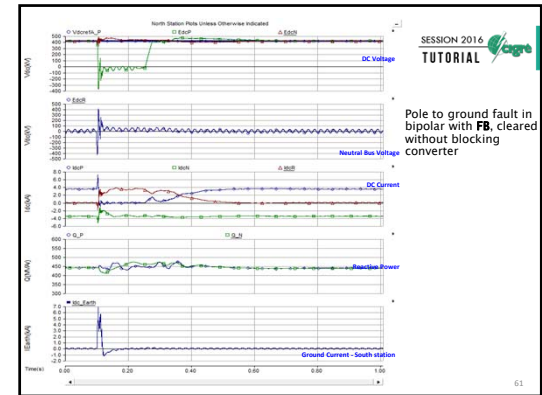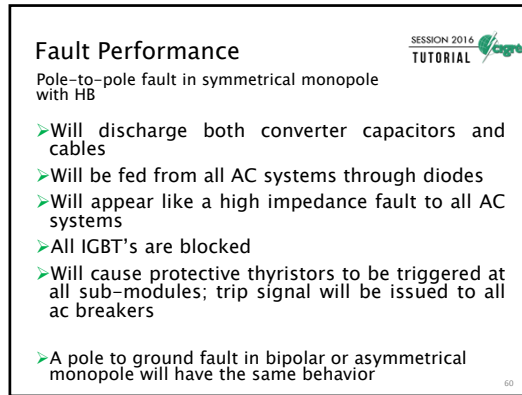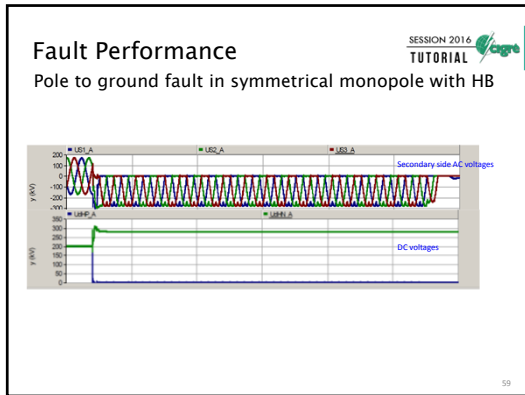


SESSION 2016
TUTORIAL 

LCC vs. VSC


Function	LCC	VSC
Semi-Conductor Device	Thyristors currently 6 inch, 8.5 kV and 5000 Amps. No controlled turn off capability	IGBTs with anti-parallel free wheeling diode, with controlled turn-off capability. Current rating 4.5 kV and turn off current of ~2000 Amps
DC transmission voltage	Up to +/- 800 kV bipolar operation	Up to +/- 500 kV currently limited by HVDC cable if extruded XLPE cable is used.
DC power	Currently in the range of 7000 MW per bipolar system	Currently in the range of 1000 MW per block
Reactive Power requirements	Consumes up to 60% of its rating reactive power	Does not consume any reactive power and each terminal can independently control its reactive power.
Filtering	Requires large filter banks	Requires moderate size filter banks or no filters at all.
Black start	Limited application	Capable of black start and feeding passive loads
AC system short circuit level	Critical in the design	Not critical at all

62

SESSION 2016
TUTORIAL 

LCC vs. VSC


Function	LCC	VSC
Commutation failure performance	Fails commutation for ac disturbances	Does not fail commutation
Over load capability	Available if designed for up to any required design value	Requires increased rating of the link
Application with overhead lines	Can be applied and dc line faults can be cleared by converter control	Can be applied but dc line faults are cleared by trip of ac breaker, or the use of a dc circuit breaker. It has mostly been applied with cables
Small taps	Not economic and affects the performance	Economic and seems not affect the performance
Load rejection over voltage	Large and has to be mitigated because of the large reactive power support	not large because of small size of filters if required.


SESSION 2016
TUTORIAL 

LCC vs. VSC

Function	LCC	VSC
Foot print	Can be large	Small for the comparable rating to an LCC
Off shore wind farms	Hard to apply	Straight forward application
Power losses	Typically 0.8% per converter station at rated power	Typically 1% per terminal

DC Grid


SESSION 2016
TUTORIAL 

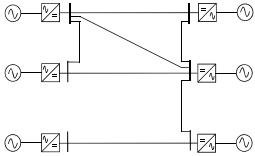

- made up of a combination of meshed and radial lines (has at least one mesh)

65


DC Grid

SESSION 2016
TUTORIAL 

- Motivated by
 - Ever increasing HVDC links
 - Need for integration of renewable generation, especially offshore wind
 - Congested right of way and need for cable transmission
 - Extra flexibility and reliability compared to point to point HVDC

66

DC Grid


SESSION 2016
TUTORIAL 

Challenges

- Need for very fast protection
- Need for fast DC breaker
- Power flow and voltage control
- Need for DC/DC converters
- Standarization
- High voltage cables
- DC grid code

67

Cigre' HVDC Activities

SESSION 2016
TUTORIAL 

- Cigre' study committee B4:
 - Global leader in HVDC and FACTS
 - Over 70 working groups, 16 ongoing, covering:
 - All technical challenges of DC grid
 - LCC and VSC HVDC equipment
 - Ground electrodes
 - Harmonic filtering
 - AC/DC interactions
 - Modeling and simulation
 -

68



COPYRIGHT & DISCLAIMER NOTICE

COPYRIGHT © 2016

This tutorial has been prepared based upon the work of CIGRE and its Working Groups. If it is used in total or in part, proper reference and credit should be given to CIGRE.

DISCLAIMER NOTICE

“CIGRE gives no warranty or assurance about the contents of this publication, nor does it accept any responsibility, as to the accuracy or exhaustiveness of the information. All implied warranties and conditions are excluded to the maximum extent permitted by law”.